

Latches and Flip-flops

CS207 Lecture 7

James YU

Apr. 1, 2020



Sequential logic

- Logic circuits for digital systems:
 - combinational logic (previous lectures),
 - sequential logic.
- Combinational?
 - Output determined by the combination of inputs.
 - Perform an operation specified by a set (combination) of Boolean functions.


Sequential logic

- Almost all electronic consumer products
 - send, receive, store, retrieve, and process information
 - depends on the ability to store binary — has memory.
- Sequential circuits
 - act as storage elements.
- The logic circuits whose outputs at any instant of time depend on the **present inputs** as well as on the **past outputs** are called *sequential circuits*.



Sequential logic

- The logic circuits whose outputs at any instant of time depend on the **present inputs** as well as on the **past outputs** are called *sequential circuits*.
- A combinational circuit, but with
 - memory elements connected in a feedback path.
 - Outputs are binary functions of not only inputs, but also the present state of the circuit.
 - A memory element is a medium in which one bit of information (0 or 1) can be stored or retained until necessary, and thereafter its contents can be replaced by a new value.

 

Sequential logic

- Sequential circuits are broadly classified into two main categories, known as
 - *synchronous* or *clocked sequential circuits*, and
 - *asynchronous* or *unclocked sequential circuits*,
 - depending on the timing of their signals.
- A sequential circuit whose behavior can be defined from **the knowledge of its signal at discrete instants of time** is referred to as a synchronous sequential circuit.
 - The synchronization is achieved by a timing device known as a system clock.
 - The outputs are affected only with the application of a clock pulse.
- A sequential circuit whose behavior **depends upon the sequence in which the input signals change** is referred to as an asynchronous sequential circuit.




Sequential logic

- A sequential circuit whose behavior can be defined from **the knowledge of its signal at discrete instants of time** is referred to as a synchronous sequential circuit.
 - The synchronization is achieved by a timing device known as a system clock.
 - The outputs are affected only with the application of a clock pulse.
- Clock pulse: when changes will happen; Other signals: what changes will happen.
- Clocked sequential circuits:
 - Synchronous sequential circuits that use clock to control.
 - Synchronous because the circuit activity and the updating of storage are synchronized.




Sequential logic

 - Memory element: *flip-flop*.
 - A binary storage device storing one bit;
 - Change in state happens only during clock pulse transition;
 - Loop cut when clock is inactive, no update.



Flip-flops

 - It can have only two states, either the 1 state or the 0 state.
- The general block diagram representation of a flip-flop is shown below:




- It has one or more inputs and two outputs.
- The two outputs are complementary to each other.
- Normally, the state of Q is called the *state* of the flip-flop, whereas the state of Q' is called the *complementary state* of the flip-flop.




Flip-flops

- There has always been considerable confusion over the use of the terms *latch* and *flip-flop*.
 - A *flip-flop* is a device which changes its state at times when a change is taking place in the clock signal.
 - An *asynchronous latch* is continuously monitoring the input signals and changes its state at times when an input signal is changing.
 - A *synchronous latch* is continuously monitoring the input signals, but only can changes its state when a control signal is active.

 

SR latches

 - By cross coupling a pair of NOR gates, we have a first latch: *SR latch*.




- The set and reset inputs are labelled S and R respectively.
- The *state table* of SR latch is shown below

Present			Next
S_t	R_t	Q_t	Q_{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	Forbidden	



SR latches

- From the k-map: $Q_{t+1} = S + R'Q$.

 


RQ

	00	01	11	10
0		1		
1	1	1	X	X


S

- A more conventional form:

 

Controlled SR latch

 - The transparency of SR latches can be controlled by an additional signal G :




- If $G = 0$, the outputs of first-level NAND gates are always **1**, disabling any changes in the second level gates.
- If G makes a transition from **0** to **1**, the first-level NAND gates are enabled, making the latch active.
- A problem with SR latches: **state is indeterminate when S and R are both 1.**



Controlled D latch

 - D latch is designed to handle this problem.
 - Also called *transparent latch*, D for data.
 - Ensure the previous S and R are never equal to 1 at the same time.



Present		Next
D_t	Q_t	Q_{t+1}
0	0	0
0	1	0
1	0	1
1	1	1




Controlled D latch

- The controlled D latch has the advantage that it only requires one data input and there is no input condition that has to be avoided.
- Transparent?
 - Data input is transferred to Q output when enable is asserted. The output follows the input.
 - When enable is de-asserted, the information is stored.




Latches

 



Flip-flops

 - Latch or flip-flop state change by a control input.
 - The event is called trigger.
- When latches are memories, difficulty arises:
 - State changes as soon as clock switches to 1.
 - Infinite loop during clock-1.



JK flip-flop

  - Latch circuits are not suitable for operation in synchronous sequential circuits because of their transparency.
 - Flip-flops are used as the basic memory elements, which only respond to a transition on a clock input.
 - A typical example is called JK flip-flop (JKFF).




Present			Next
J_t	K_t	Q_t	Q_{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0



JK flip-flop

 - J is S , and K is R .
- When $J = K = 1$, the flip-flop **toggles**.
- Combining the two AND gates with the SR latch circuit, we have the following reduced circuit:




- However, the above circuit alone still cannot resolve the problem with latches.
 - A master-slave JKFF can be used.



JK flip-flop

 - The master-slave JKFF consists of two SR latches, the master and the slave.
 - The master is clocked in the normal way, while the slave clock is inverted:



- When the clock is 1, the master latch works transparently.
 - However, as the slave latch is disabled at the same time, no changes will be reflected on the output.
- Upon the clock is changed to 0, the slave is activated to reflect the data from master to the output.
 - However, the master latch is disabled: no further changes on input will be reflected.




Asynchronous control

- As well as the J , K , and clock inputs, a master-slave JKFF may also have one or two additional controls to set the state of flip-flop irrespective of clock:
 - These asynchronous controls are usually called *preset* and *clear*.

Cl	Pr	Q
1	1	Forbidden
1	0	0
0	1	1
0	0	X


- If $Cl = 1$ and $Pr = 0$ both master and slave are cleared to 0.
- If $Cl = 0$ and $Pr = 1$ the flip-flop is preset to 1.
- Active high on Cl and Pr will override J and K .

Asynchronous control

 


D flip-flop

 - A negative edge triggered D type master-slave FF consists of a pair of D latches:




 - Right is the symbolic diagram of DFF.
- The triangle is termed *dynamic input indicator*.



D flip-flop


 
- An alternative configuration of a DFF consists of three pairs of cross-coupled NAND gates, each pair constituting a basic S'R' latch:



- The latch is stable when $S' = R' = 1, Q = 0$.
- To change the state, S' must make a $1 \rightarrow 0$ transition.





D flip-flop

  

JK flip-flop revisit

  - The previous DFF can be modified to provide the function of a JKFF as follows:





- If $J = K = 1$ and $Q' = 1$, the input to DFF is 1, the Q outputs 1.
- Think what happens when $J = 1$ and $K = 0$, and vice versa.




T flip-flop

  - Finally, a T flip-flop toggles the state when input $T = 1$ upon clock signal.
- It is simple to construct a TFF from JKFF:



- or DFF:

 

Characteristic table

- A *characteristic table* describes the logical properties of a flip-flop by describing its operation in tabular form.

J	K	Q_{t+1}	
0	0	Q_t	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'_t	Complement

D	Q_{t+1}	
0	0	Reset
1	1	Set

T	Q_{t+1}	
0	Q_t	No change
1	Q'_t	Complement



Characteristic equation

- A characteristic equation describes the logical properties of a flip-flop by describing its Boolean function.
- JKFF: $Q_{t+1} = D$.
- DFF: $Q_{t+1} = JQ'_t + K'Q_t$.
- TFF: $Q_{t+1} = T \oplus Q_t$.

J	K	Q_{t+1}	
0	0	Q_t	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'_t	Complement

D	Q_{t+1}	
0	0	Reset
1	1	Set

T	Q_{t+1}	
0	Q_t	No change
1	Q'_t	Complement



Verilog: Parameters

- Let's assume that we have a design which requires us to have counters of various width, but with the same functionality.
 - Normally what we do is creating counters of different widths and then use them.
- Verilog provides a powerful way to overcome this problem: it provides us with something called *parameter*.
 - These parameters are like constants local to that particular module.
- We can override the default values, either using `defparam` or by passing a new set of parameters during instantiation.
 - We call this *parameter overriding*.

Verilog: Parameters

- A parameter is defined by Verilog as a constant value declared within the module structure.
- The value can be used to define a set of attributes for the module which can characterize its behavior as well as its physical representation.
 - Defined inside a module.
 - Local scope.
 - Maybe overridden at instantiation time.
 - If multiple parameters are defined, they must be overridden in the order they were defined.
 - If an overriding value is not specified, the default parameter declaration values are used.
- Maybe changed using the `defparam` statement.

Verilog: Parameters

```
1 module secret_number;  
2   parameter my_secret = 0;  
3  
4   initial begin  
5     $display("My secret number is %d", my_secret);  
6   end  
7 endmodule  
8  
9 module defparam_example();  
10  defparam U0.my_secret = 11;  
11  defparam U1.my_secret = 22;  
12  
13  secret_number U0();  
14  secret_number U1();  
15 endmodule
```



Verilog: Parameters

```
1 module secret_number;  
2   parameter my_secret = 0;  
3  
4   initial begin  
5     $display("My secret number in module is %d", my_secret);  
6   end  
7 endmodule  
8  
9 module param_override_instance_example();  
10  
11   secret_number #(11) U0();  
12   secret_number #(22) U1();  
13 endmodule
```



Verilog: Parameters

```
1 module ram_sp_sr_sw (  
2     clk      , // Clock Input  
3     address  , // Address Input  
4     data     , // Data  
5     cs       , // Chip Select  
6     we       , // Enable  
7     oe       // Output En  
8 );  
9  
10 parameter DATA_WIDTH = 8 ;  
11 parameter ADDR_WIDTH  = 8 ;  
12 parameter RAM_DEPTH  = 1 <<  
13     ADDR_WIDTH;  
14 // Actual code of RAM here  
15 endmodule
```

```
1 module ram_controller ();  
2  
3 // Controller Code  
4  
5 ram_sp_sr_sw #(16,8,256) ram(  
6     clk,address,data,cs,we,oe);  
7  
8 endmodule
```

