

Boolean Algebra and Logic Gates

CS207 Lecture 2

James YU

Feb. 26, 2020



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY

Binary logic

- Binary logic deals with variables that take on two discrete values and with logical operations.
- Three basic logical operations:
 - **AND**: $x \cdot y = z$ or $xy = z$.
 - **OR**: $x + y = z$.
 - **NOT**: $x' = z$

AND			OR			NOT	
x	y	$x \cdot y$	x	y	$x + y$	x	x'
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		



Boolean Algebra

- The previous binary logic is *two-valued Boolean algebra*.
 - On a set of two elements: 0 and 1.
 - With rules for the three binary operators: +, · and '.
- Common properties:
 - $A + 0 = A$ and $A \cdot 1 = A$.
 - $A + 1 = 1$ and $A \cdot 0 = 0$.
 - $A + A' = 1$ and $A \cdot A' = 0$.
 - $A + A = A$ and $A \cdot A = A$.
 - $(A')' = A$.

Postulates

- **Closure:** A set S is closed with respect to a binary operator if, for every pair of elements of S , the binary operator specifies a rule for obtaining a unique element of S .
- **Associative law:** $A + (B + C) = (A + B) + C$ and $A(BC) = (AB)C$.
- **Commutative law:** $A + B = B + A$ and $AB = BA$.
- **Identity element:** A set S is to have an identity element with respect to a binary operation $*$ on S , if there exists an element $E \in S$ with the property $E * A = A * E = A$.
 - Element 0 is an identity element of $+$, and 1 is an identity element of \cdot .
- **Distributive law:** $A(B + C) = AB + AC$ and $A + BC = (A + B)(A + C)$.
- **DeMorgan:** $(A + B)' = A'B'$ and $(AB)' = A' + B'$.
- **Absorption:** $A + AB = A$ and $A(A + B) = A$.



Duality property

- Every algebraic expression deducible from the postulates of Boolean algebra remains valid if the operators and identity elements are interchanged.
- Change $+$ to \cdot and vice versa.
- Change 0 to 1 and vice versa.
 - $A + A' = 1 \rightarrow A \cdot A' = 0$.
 - $A + B = B + A \rightarrow AB = BA$.
 - $A(B + C) = AB + AC \rightarrow A + BC = (A + B)(A + C)$.
 - $(A + B)' = A'B' \rightarrow (AB)' = A' + B'$.



Boolean function

- Binary variables have two values, either 0 or 1.
- A Boolean function is an expression formed with *binary variables*, the two *binary operators* **AND** and **OR**, one *unary operator* **NOT**, *parentheses* and *equal sign*.
- The value of a function may be 0 or 1, depending on the values of variables present in the Boolean function or expression.
- Example: $F = AB'C$.
 - $F = 1$ when $A = C = 1$ and $B = 0$,
 - otherwise $F = 0$.

Boolean function

- Boolean functions can also be represented by truth tables.
 - Tabular form of the values of a Boolean function according to the all possible values of its variables.
- n number of variables $\rightarrow 2^n$ combinations of 1's and 0's
- One column representing function values according to the different combinations.
- Example: $F = AB + C$.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



Boolean function simplification

- A Boolean function from an algebraic expression can be realized to a logic diagram composed of logic gates.
- Minimization of the number of literals and the number of terms leads to less complex circuits as well as less number of gates.
 - We first try use postulates and theorems of Boolean algebra to simplify.

$$\begin{aligned}F &= AB + BC + B'C \\&= AB + C(B + B') \\&= AB + C\end{aligned}$$

$$\begin{aligned}F &= A'B'C + A'BC + AB' \\&= A'C(B' + B) + AB' \\&= A'C + AB'\end{aligned}$$

$$\begin{aligned}F &= XYZ + XY'Z + XYZ' \\&= XZ(Y + Y') + XY(Z + Z') \\&= XZ + XY = X(Y + Z)\end{aligned}$$

- Each Boolean function has one representation in truth table, but a variety of ways in algebraic form.



Algebraic manipulation

- Reduce the total number of terms and literals.
- Usually not possible by hand for complex functions, use computer minimization program.
- More advanced techniques in the next lectures.

Boolean function complement

- Complement a Boolean function from F to F' .
 - Change 0's to 1's and vice versa in the truth table.
 - Use DeMorgan's theorem for multiple variables.
- Example: $F = x'yz' + x'y'z$.

Complement:

$$\begin{aligned}F' &= (x'yz' + x'y'z)' \\&= (x'yz')'(x'y'z)' \\&= (x + y' + z)(x + y + z')\end{aligned}$$

Dual:

$$F^* = (x' + y + z')(x' + y' + z)$$

Canonical forms

- Logical functions are generally expressed in terms of different combinations of logical variables with their true forms as well as the complement forms: x and x' .
- An arbitrary logic function can be expressed in the following forms, called *canonical forms*:
 - *Sum of products* (SOP), and
 - *Product of sums* (POS).
- What are the products and sums?



Canonical forms

- The logical product of several variables on which a function depends is considered to be a product term.
 - Called **minterms** when all variables are involved: For x and y , xy , $x'y$, xy' , and $x'y'$ are all the minterms.
- The logical sum of several variables on which a function depends is considered to be a sum term.
 - Called **maxterms** when all variables are involved: For x and y , $x + y$, $x' + y$, $x + y'$, and $x' + y'$ are all the maxterms.
- **SOP**: The logical sum of two or more logical product terms is referred to as a sum of products expression.
- **POS**: The logical product of two or more logical sum terms is referred to as a product of sums expression.



Minterms

- In the minterm, a variable will possess the value **1** if it is in true or uncomplemented form, whereas, it contains the value **0** if it is in complemented form.

<i>A</i>	<i>B</i>	<i>C</i>	Minterm
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	ABC'
1	1	1	ABC

- It possesses the value of **1** for only one combination of n input variables
 - The rest of the $2^n - 1$ combinations have the logic value of **0**.



Minterms

- **Canonical SOP** expression, or **sum of minterms**: A Boolean function expressed as the logical sum of all the minterms from the rows of a truth table with value 1.

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>	Minterms
0	0	0	0	$A'B'C'$
0	0	1	1	$A'B'C$
0	1	0	0	$A'BC'$
0	1	1	1	$A'BC$
1	0	0	0	$AB'C'$
1	0	1	1	$AB'C$
1	1	0	1	ABC'
1	1	1	1	ABC

- $F = AB + C = A'B'C + A'BC + AB'C + ABC' + ABC = \sum(1, 3, 5, 6, 7)$.
 - A compact form by listing the corresponding decimal-equivalent codes of the minterms.



Minterms

- The canonical sum of products form of a logic function can be obtained by using the following procedure.
 - ① Check each term in the given logic function. Retain if it is a minterm, continue to examine the next term in the same manner.
 - ② Examine for the variables that are missing in each product which is not a minterm.
 - ③ If the missing variable in the minterm is X , multiply that minterm with $(X + X')$.
 - Example: $A + B \rightarrow A(B + B') + B(A + A')$
 - ④ Multiply all the products and discard the redundant terms.



Minterms

- Example: $F(A, B, C, D) = AB + ACD$.

$$\begin{aligned}F(A, B, C, D) &= AB + ACD \\&= AB(C + C')(D + D') + ACD(B + B') \\&= (ABC + ABC')(D + D') + ABCD + AB'CD \\&= ABCD + ABCD' + ABC'D + ABC'D' + ABCD + AB'CD \\&= ABCD + ABCD' + ABC'D + ABC'D' + AB'CD\end{aligned}$$



Maxterms

- In the maxterm, a variable will possess the value 0, if it is in true or uncomplemented form, whereas, it contains the value 1, if it is in complemented form.

<i>A</i>	<i>B</i>	<i>C</i>	Maxterm
0	0	0	$A + B + C$
0	0	1	$A + B + C'$
0	1	0	$A + B' + C$
0	1	1	$A + B' + C'$
1	0	0	$A' + B + C$
1	0	1	$A' + B + C'$
1	1	0	$A' + B' + C$
1	1	1	$A' + B' + C'$

- It possesses the value of 0 for only one combination of n input variables
 - The rest of the $2^n - 1$ combinations have the logic value of 1.



Maxterms

- *Canonical POS* expression, or *product of maxterms*: A Boolean function expressed as the logical product of all the maxterms from the rows of a truth table with value 0.
- $F = (A + B + C)(A + B' + C)(A' + B + C') = \prod(0, 2, 5)$.
 - A compact form by listing the corresponding decimal-equivalent codes of the maxterms.

Maxterms

- Example: $F(A, B, C, D) = A + B'C$.

$$F(A, B, C, D) = A + B'C$$

$$= (A + B')(A + C)$$

$$= (A + B' + CC')(A + C + BB')$$

$$= (A + B' + C)(A + B' + C')(A + B + C)(A + B' + C)$$

using the distributive property: $X + YZ = (X + Y)(X + Z)$

$$= (A + B' + C)(A + B' + C')(A + B + C)$$



Derive from a truth table

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>	Minterm	Maxterm
0	0	0	0		$A + B + C$
0	0	1	0		$A + B + C'$
0	1	0	1	$A'BC'$	
0	1	1	0		$A + B' + C'$
1	0	0	1	$AB'C'$	
1	0	1	1	$AB'C$	
1	1	0	1	ABC'	
1	1	1	0		$A' + B' + C'$

- The final **canonical SOP** for the output F is derived by summing or performing an **OR** operation of the four product terms as shown below:
 - $F = A'BC' + AB'C' + AB'C + ABC' = \sum(2, 4, 5, 6).$
- The final **canonical POS** for the output F is derived by summing or performing an **AND** operation of the four sum terms as shown below:
 - $F = (A + B + C)(A + B + C')(A + B' + C')(A' + B' + C') = \prod(0, 1, 3, 7).$



Conversion between minterms and maxterms

- Minterms are the complement of corresponding maxterms: $m_i = M_i'$.
 - Example: $A' + B' + C' = (ABC)'$.

$$\begin{aligned}F(A, B, C) &= \sum(2, 4, 5, 6) = m_2 + m_4 + m_5 + m_6 \\&= A'BC' + AB'C' + AB'C + ABC'\end{aligned}$$

$$F'(A, B, C) = \sum(0, 1, 3, 7) = m_0 + m_1 + m_3 + m_7$$

$$\begin{aligned}F(A, B, C) &= (F'(A, B, C))' = (m_0 + m_1 + m_3 + m_7)' \\&= m_0' m_1' m_3' m_7' \\&= M_0 M_1 M_3 M_7 \\&= \prod(0, 1, 3, 7) \\&= (A + B + C)(A + B + C')(A + B' + C')(A' + B' + C').\end{aligned}$$



Other logic operators

- When the binary operators AND and OR are applied on two variables A and B , they form two Boolean functions AB and $A + B$ respectively.



Other logic operators

- When the three operators AND, OR, and NOT are applied on two variables A and B , they form 16 Boolean functions:

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x , but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y , but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \subset y$	Implication	If y , then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1







Digital logic gates

- As Boolean functions are expressed in terms of AND, OR, and NOT operations, it is easier to implement the Boolean functions with these basic types of gates.
 - It is possible to construct other types of logic gates.
- The following factors are to be considered for construction of other types of gates.
 - The **feasibility** and economy of producing the gate with physical parameters.
 - The possibility of **extending** to more than two inputs.
 - The basic properties of the binary operator such as **commutability** and **associability**.
 - The ability of the gate to **implement Boolean functions** alone or in conjunction with other gates.

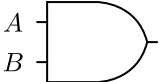
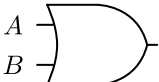



Digital logic gates

		A	B	F
AND	 $F = AB$	0	0	0
		0	1	0
		1	0	0
		1	1	1
OR	 $F = A + B$	0	0	0
		0	1	1
		1	0	1
		1	1	1
NOT	 $F = A'$	0	-	1
		1	-	0
Buffer	 $F = A$	0	-	0
		1	-	1







Digital logic gates

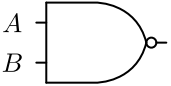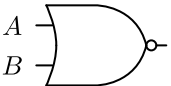	A	B	F
NAND  $F = (AB)'$	0	0	1
	0	1	1
	1	0	1
	1	1	0
NOR  $F = (A + B)'$	0	0	1
	0	1	0
	1	0	0
	1	1	0
XOR  $F = AB' + A'B$ $= A \oplus B$	0	0	0
	0	1	1
	1	0	1
	1	1	0





Multiple input logic gates

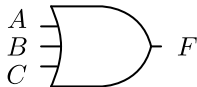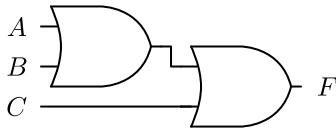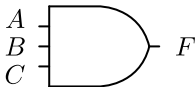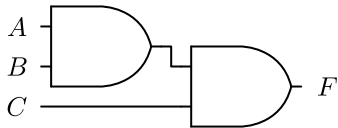- A gate can be extended to have multiple inputs if its binary operation is commutative and associative.
- AND and OR gates are both commutative and associative.
 - $F = ABC = (AB)C$.
 - $F = A + B + C = (A + B) + C$.





Multiple input logic gates

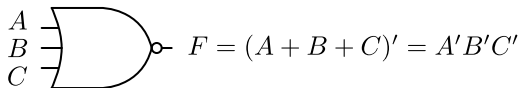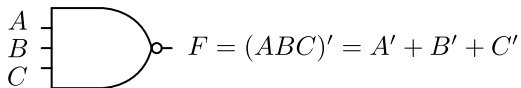- The NAND and NOR functions are the complements of AND and OR functions respectively.
 - They are commutative, but **not associative**.
 - $((AB)'C)' \neq (A(BC)')'$: does not follow associativity.
 - $((A + B)' + C)' \neq (A + (B + C)')'$: does not follow associativity.
- We modify the definition of multi-input NAND and NOR:






Multiple input logic gates

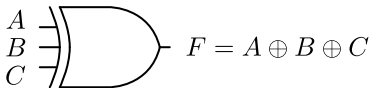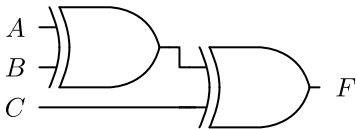- The XOR gates and equivalence gates both possess commutative and associative properties.
 - Gate output is low when even numbers of 1's are applied to the inputs, and when the number of 1's is odd the output is logic 0.
 - Multiple-input exclusive-OR and equivalence gates are uncommon in practice.





Universal gates

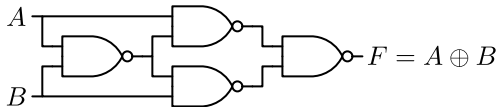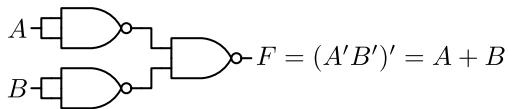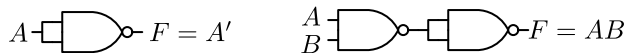- NAND gates and NOR gates are called *universal gates* or *universal building blocks*.
- Any type of gates or logic functions can be implemented by these gates.



Universal gates

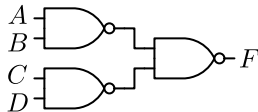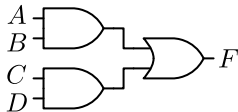- Universal gates are easier to fabricate with electronic components.
 - Also reduce the number of varieties of gates.
- Example: $F = AB + CD$ requires two AND and one OR gates.
 - Or three NAND gates.
 - $F = AB + CD = ((AB + CD)')' = ((AB)'(CD)')'$



Verilog

- Verilog is a hardware Description Language (HDL) that consists of digital logic. It is intended to be used for simulations, timing analysis, testing, and synthesis.
- The basic building block of Verilog is the module statement.

```
1 module <module_name>(<input_list>, <output_list>);  
2 input <input_list>;  
3 output <output_list>;  
4  
5 endmodule
```


Verilog modules

- Example: A module that takes in three inputs: two 5-bit operands called `a` and `b`, and an enable input called `en`.

```
1 module comparator(a, b, en, a_gt_b);  
2   input [4:0] a, b;  
3   input en;  
4   output a_gt_b;  
5  
6 endmodule
```

- In this state, the module just does nothing, for two reasons.
 - There is no code in the body of the module.
 - defining a module in and of itself does nothing (unless it is the top level module).
 - We need to create an instance of a module in our design to actually use it.

Instantiating modules

- We can include an instance of a module within another module using the following syntax:

```
1 <module_name> <instance_name>(<port_list>);
```

- Example: to instantiate a comparator module with the name `comp1`, input wires `in1`, `in2`, and `en`, and an output wire `gt`, we could write:

```
1 comparator comp1(in1, in2, en, gt);
```

- This instantiation depends on the ordering of the ports in the comparator module.



Instantiating modules

- There is an alternate syntax for instantiating modules which does not depend on port ordering:

```
1 <module_name> <instance_name>(<port_name>(ioname), ...);
```

- Continuing from the last example, we could instead write:

```
1 comparator comp1(.b(in2), .a(in1), .en(en), .a_gt_b(gt));
```

```
1 comparator comp1(in1, in2, en, gt);
```

Comments

- Comments in Verilog are exactly the same as in Java.

```
1 // This is a comment  
2 /* Multi-line  
3    comment */
```



Numerical

- Many modules will contain numerical literals.
- In Verilog, numerical literals are unsigned 32-bit numbers by default.
- You should get into the habit of declaring the width of each numerical literal.

```
1 /* General syntax:
2    <bits>'<base><number>
3    where <base> is generally b, d, or h */
4
5 wire [2:0] a = 3'b111; // 3 bit binary
6 wire [4:0] b = 5'd31; // 5 bit decimal
7 wire [31:0] c = 32'hdeadbeef; // 32 bit hexadecimal
```

Constants

- We can use ``define` to define global constants in our code.
 - **Do not append a semicolon** to the ``define` statement.

```
1 `define RED 2'b00 // DON'T add a semicolon to these statements
2 `define WHITE 2'b01
3 `define BLUE 2'b10
4
5 wire [1:0] color1 = `RED;
6 wire [1:0] color2 = `WHITE;
7 wire [1:0] color3 = `BLUE;
```

Wires

- To start with, we have two kinds of data types in our modules: *wires* and *registers*.
- You can think of *wires* as modeling physical wires.

```
1 wire      a_wire;  
2 wire [1:0] two_bit_wire;  
3 wire [4:0] five_bit_wire;
```

Wires

- We then use the `assign` statement to connect them to something else.
 - Assume that we are in a module that takes a two bit input named `two_bit_input`:

```
1 wire      a_wire;
2 wire [1:0] two_bit_wire;
3 wire [4:0] five_bit_wire;
4
5 assign two_bit_wire = two_bit_input;
6 // Connect a_wire to the lowest bit of two_bit_wire
7 assign a_wire = two_bit_wire[0];
8 /* {} is concatenation - 3 MSB will be 101, 2 LSB will be
9 connected to two_bit_wire */
10 assign five_bit_wire = {3'b101, two_bit_wire};
11 // This is an error! You cannot assign a wire twice!
12 // assign a_wire = 1'b1;
```



Wires

- There is a shortcut that is sometimes used to declare and assign a wire at the same time:

```
1 // Declares gnd, and assigns it to 0  
2 wire gnd = 1'b0;
```