

Synchronous Sequential Logic I

CS207 Lecture 9

James YU

Apr. 15, 2020



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY


Analysis of clocked sequential circuits

- Describes what a given circuit will do under certain operating conditions.
 - Obtaining a table or a diagram for the time sequence of inputs, outputs, and internal states.
 - Or obtain the Boolean expressions that describes the behavior of the circuit.
- A diagram is a clock sequential circuit, if it includes flip-flops and clock inputs.




Analysis of clocked sequential circuits

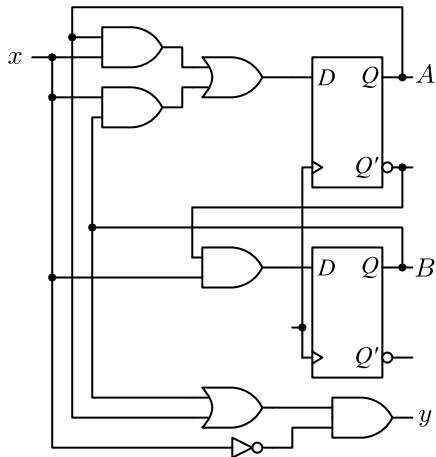- The behavior can be described with state equations, or transition equations.



Analysis of clocked sequential circuits

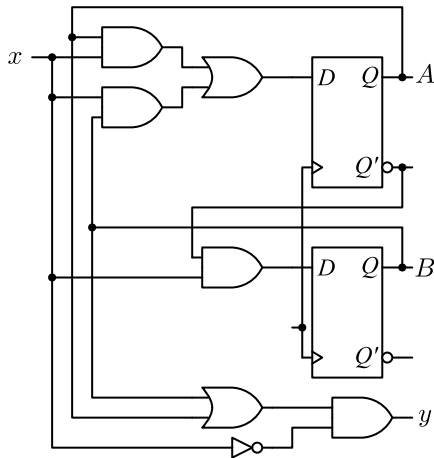
- Two D flip-flops:
 - $A(t+1) = A(t)x(t) + B(t)x(t)$,
 - $B(t+1) = A'(t)x(t)$.
- The output:
 - $y(t) = [A(t) + B(t)]x(t)'$.
 - Since all signals are labeled by t , we can also write $y = (A + B)x'$.



Analysis of clocked sequential circuits

- Time-sequence of inputs, outputs, FFs can be enumerated in a *state table*.

Present		Input	Next		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

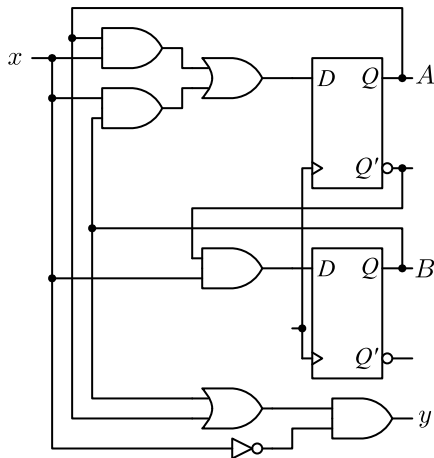

Analysis of clocked sequential circuits


- State table has 2^{m+n} rows for m flip-flops and n inputs, which is very long.
- Or with three sections, with input in the next state and output column.

Present		Next				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0



Analysis of clocked sequential circuits

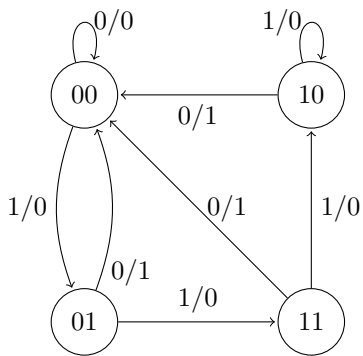- **State diagram:**
 - Each state as a circle.
 - Transitions between states are directed lines connecting the circles.




Present		Next				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0



Analysis of clocked sequential circuits

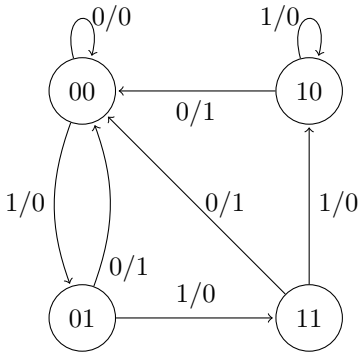- Circuit diagram \rightarrow Equations \rightarrow State table \rightarrow State diagram.
 - State table is easier to derived from circuit diagram and state equations.
 - State diagram gives a pictorial view of state transitions.
- The shown diagram is a 1-detector.



Analysis of clocked sequential circuits

- The logic diagram of a sequential circuit consists of flip-flops and gates.
- The interconnections among the gates form a combinational circuit and may be specified algebraically with Boolean expressions.
- The part of the combinational circuit that generates external outputs is described algebraically by a set of Boolean functions called *output equations*.
- The part of the circuit that generates the inputs to flip-flops is described algebraically by a set of Boolean functions called *flip-flop input equations* (or, sometimes, *excitation equations*).



Analysis of clocked sequential circuits

- We will adopt the convention of using the flip-flop input symbol to denote the input equation variable and a subscript to designate the name of the flip-flop output.
 - For example, the following input equation specifies an OR gate with inputs x and y connected to the D input of a flip-flop whose output is labeled with the symbol Q :

$$D_Q = x + y$$




Analysis of clocked sequential circuits

- The sequential circuit consists of two D flip-flops A and B , an input x , and an output y .
- The logic diagram of the circuit can be expressed algebraically with two flip-flop input equations and an output equation:

$$D_A = Ax + Bx,$$

$$D_B = A'x,$$

$$y = (A + B)x'.$$

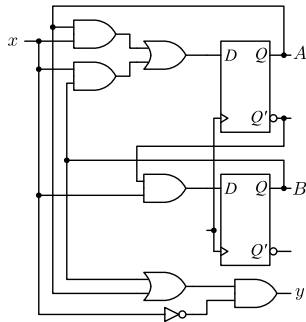

Analysis with JK/T flip-flops

- JK flip-flops and T flip-flops are different from D flip-flops whose state equation is the same as the input equation.
 - Refer to the corresponding characteristic equation.
- Next-state values can be derived by
 - Determining input equations.
 - Listing binary values for each input equation.
 - Using the corresponding flip-flop characteristic table to determine next state values.




An example

- Determine input equations:

$$J_A = B, K_A = Bx',$$

$$J_B = x' K_B = A \oplus x.$$

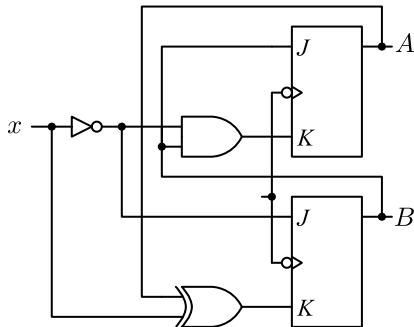

An example

- List binary values for each input equation.
- Use the corresponding flip-flop characteristic table to determine next state values.
 - $Q(t+1) = JQ' + K'Q$.
- $A(t+1) = J_A A' + K'_A A = A'B + A(Bx')'$.
- $B(t+1) = J_B B' + K'_B B = x'B + B(A \oplus x)'$.



An example


- $A(t+1) = J_A A' + K'_A A = A'B + A(Bx')'$.
- $B(t+1) = J_B B' + K'_B B = x'B + B(A \oplus x)'$.

Present		Input	Next		FF Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0



An example

Present		Input	Next		FF Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

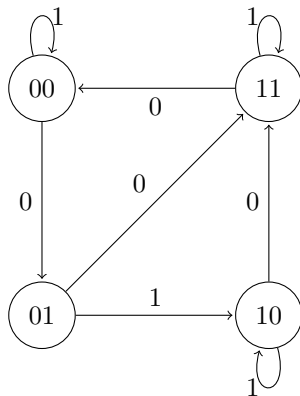


Another example

- Determine input equations:

$$T_A = Bx, T_B = x$$


$$y = AB.$$

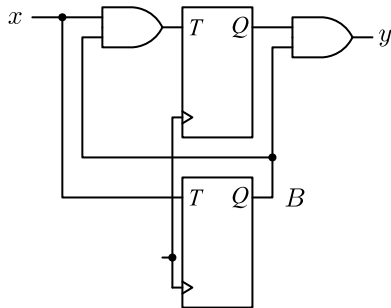- List binary values for each input equation.
- Use the corresponding flip-flop characteristic table to determine next state values.
 - $Q(t+1) = T \oplus Q = T'Q + TQ'$.
- $A(t+1) = (Bx)'A + (Bx)A' = AB' + Ax' + A'Bx.$
- $B(t+1) = x \oplus B.$




Another example

Present		Input	Next		Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

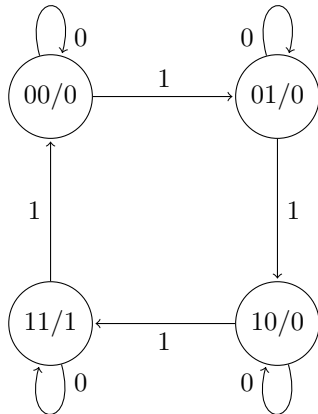

Finite state machine

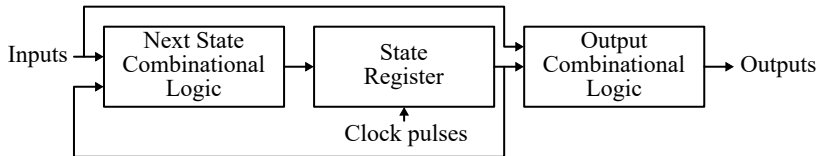- The most general model of a sequential circuit has inputs, outputs, and internal states.
- It is customary to distinguish between two models of sequential circuits:
 - *Mealy model.*



- *Moore model.*

