

Combinational Logic I

CS207 Lecture 5

James YU

Mar. 18, 2020



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY


Combinational logic

- Logic circuits for digital systems:
 - combinational logic,
 - sequential logic (next lectures).
- *Combinational?*
 - Output determined by the combination of inputs.
 - Perform an operation specified by a set (combination) of Boolean functions.




Combinational logic

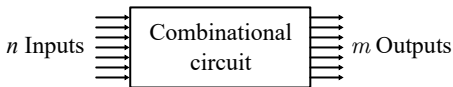- An interconnection of logic gates that
 - react to values of input signals,
 - produce output signal values,
 - n inputs from external sources, and
 - m outputs go to external destinations.



Combinational logic

 - Two representations of a combinational circuit:
 - 2^n possible input combinations: truth table, or
 - m outputs: m Boolean functions, each expressed with the n inputs.



Analysis of combinational logic


- Analysis of a combinational circuit: determine the function of the circuit.
 - Given logic diagram,
 - develop a set of Boolean functions, a truth table, an optional explanation of the circuit operation.
- If a function name or an explanation is given along the circuit, just verify if the given information is correct.

Analysis of combinational logic

- Obtain the output Boolean functions:
 - Label all gate outputs that are a function of only inputs, no other intermediate variables. Determine their Boolean functions.
 - Label all gates that are a function of inputs and the gates in the previous step. Determine their Boolean functions.
 - List output Boolean functions, squeeze the intermediate variables.

Analysis of combinational logic

 - Obtain the output Boolean functions:
 - Label all gate outputs that are a function of only inputs, no other intermediate variables. Determine their Boolean functions.




- $T_1 = A + B + C.$
- $T_2 = ABC.$
- $F_2 = AB + AC + BC.$



Analysis of combinational logic

 - Obtain the output Boolean functions:
 - Label all gates that are a function of inputs and the gates in the previous step. Determine their Boolean functions.




- $T_3 = F'_2 + T_1.$
- $F_1 = T_2 + T_3.$



Analysis of combinational logic

 - Obtain the output Boolean functions:
 - List output Boolean functions, squeeze the intermediate variables.



$$\begin{aligned}F_1 &= T_2 + T_3 \\&= ABC + F_2' T_1 \\&= ABC + \\&\quad (AB + AC + BC)' \\&\quad (A + B + C) \\&= ABC + A'B'C + \\&\quad AB'C' + A'BC'\end{aligned}$$

Analysis of combinational logic

- Truth table is simple with Boolean function
 - Determine the number of input variables. For n inputs, form the 2^n combinations from 0 to 2^n-1 .
 - Label the outputs of the intermediate gates.
 - Obtain the truth table for these outputs.
 - Obtain the truth table for the remaining outputs.

A	B	C	F_2	F_2'	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1



Design of combinational logic

- Design of a combinational circuits: develop a logic circuit diagram or a set of Boolean functions.
 - From specification of the design objective
- Involves the following steps:
 - Determine required number of inputs and outputs.
 - Derive the truth table.
 - Obtain simplified Boolean function for each output.
 - Draw logic diagram and verify the correctness.



Design of combinational logic

- Example: Convert from BCD decimal code to excess-3 code.

Input BCD				Output Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

- Obviously, four inputs and four outputs
- And we already have the truth table
- Then the Boolean functions.
How?
 - Remember K-maps?



Design of combinational logic

$$w = A + BC + BD$$

CD

		00	01	11	10
00		0	0	0	0
01		0	1	1	1
11		X	X	X	X
10		1	1	X	X

$$x = B'C + B'D + BC'D'$$

CD

		00	01	11	10
00		0	1	1	1
01		1	0	0	1
11		X	X	X	X
10		0	1	X	X



Design of combinational logic

$$y = CD + C'D'$$

		CD			
		00	01	11	10
AB	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

$$z = D'$$

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	0	0	1
	11	X	X	X	X
	10	1	0	X	X




Design of combinational logic

- We manipulate these Boolean functions to reuse common gates:
 - $w = A + BC + BD = A + B(C + D)$.
 - $x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$.
 - $y = CD + C'D' = CD + (C + D)'$.
 - $z = D'$.



Design of combinational logic

 


Combinational logic design with MSI circuits

- Since the introduction of MSI and LSI circuits, the traditional methods of logic design have largely been superseded.
 - Traditionally, the design engineer has developed a Boolean equation as the solution to a particular problem.
 - This function has then been minimised and implemented using SSI circuits.
- In practice, many combinational circuits may have a large number of inputs and outputs.
 - Consequently the use of truth tables in the design of such circuits is impractical.
- The development of MSI circuits has led to the technique of splitting a complex design into a number of sub-systems.



Multiplexer

 
- A multiplexer (MUX) selects 1-out-of- n lines where n is usually 2, 4, 8, or 16.
- A block diagram of a multiplexer having four input data lines d_0 , d_1 , d_2 , and d_3 and complementary outputs f and f' .



Multiplexer


- The device has two control or selection lines A and B and an enable line E .
- The characteristic equation of the multiplexer is
 
$$f = A'B'd_0 + A'Bd_1 + AB'd_2 + ABd_3.$$




Interconnecting multiplexers

 - Data within a digital system is normally processed in parallel form in order to increase the speed of operation.
- If the output of the system has to be transmitted over a relatively long distance then a parallel-to-serial conversion will take place.
- Example: An 8-bit word is presented in parallel at the data inputs.



Interconnecting multiplexers

 
- The principle of data selection can be extended to allow the selection of 1-out-of-64 lines.
 - Using nine 8-to-1 multiplexers arranged in two levels of multiplexing.



Multiplexer as a Boolean function generator

- For a 4-to-1 MUX the characteristic equation is $f = A'B'd_0 + A'Bd_1 + AB'd_2 + ABd_3$.
 - A and B are Boolean variables, applied at the select inputs, which can be factored out of any Boolean function of n variables.
 - The remaining $n - 2$ variables, referred to as the *residue variables*, can be formed into residue functions which can then be applied at the data inputs.
- Example: $f(A, B, C) = \sum(0, 1, 3, 4, 7)$.

		BC			
		00	01	11	10
A	0	1	1	1	
	1	1		1	

 


Multiplexer as a Boolean function generator

- Example: $f(A, B, C, D) = \sum(0, 1, 3, 4, 5, 9, 10, 11, 14, 15)$.


A	B	C	D	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0

...

 


Demultiplexer

 - As the name infers, a demultiplexer performs the opposite function to that of a multiplexer.
 - A single data line can be connected to any one of the output lines provided by the choice of an appropriate select signal.
 - If there are s select inputs then the number of output lines to which the data can be routed is $n = 2^s$.



Multiplexer/demultiplexer data transmission system

- A simple data transmission system can be implemented using a multiplexer and a demultiplexer in conjunction with an interconnecting single line link.
 - Such a system used over a relatively short distance such as 500 metres can result in a significant reduction in the number of lines required to transmit the data.
 - The data presented in parallel at the MUX inputs is converted into a serial format for transmission.
 - At the receiving end the demultiplexer routes the serial data, in the correct sequence, to one of the eight output lines.

 

Verilog: Control statements

- Similar to Java, Verilog has the following control statements:
 - `if-else`
 - `case`
 - `forever`
 - `repeat`
 - `while`
 - `for` loop



The conditional statement **if-else**

- The **if-else** statement controls the execution of other statements. In programming language like Java, **if-else** controls the flow of program.
 - When more than one statement needs to be executed for an **if** condition, then we need to use **begin** and **end** as seen in earlier examples.
- Syntax:

```
1 if (condition)
2   statements;
```

```
1 if (condition)
2   statements;
3 else
4   statements;
```

```
1 if (condition)
2   statements;
3 else if (condition)
4   statements;
5 ...
6 else
7   statements;
```



The conditional statement `if-else`

```
1 module if_else();  
2   reg dff;  
3   wire clk,din,reset;  
4  
5   always @ (posedge clk)  
6     if (reset) begin  
7       dff <= 0;  
8     end else begin  
9       dff <= din;  
10    end  
11 endmodule
```



The conditional statement `case`

```
1 module mux (a,b,c,d,sel,y);  
2   input a, b, c, d;  
3   input [1:0] sel;  
4   output y;  
5   reg y;  
6  
7   always @ (a or b or c or d or sel)  
8   case (sel)  
9     0 : y = a;  
10    1 : y = b;  
11    2 : y = c;  
12    3 : y = d;  
13    default : $display("Error in SEL");  
14 endcase  
15 endmodule
```



The conditional statement `case`

```
1 module mux (a,b,c,d,sel,y);
2   input a, b, c, d;
3   input [1:0] sel;
4   output y;
5   reg y;
6
7   always @ (a or b or c or d or sel)
8     case (sel)
9       0 : y = a;
10      1 : y = b;
11      2 : y = c;
12      3 : y = d;
13      2'bxx,2'bx0,2'bx1,2'b0x,2'b1x,
14      2'bzz,2'bz0,2'bz1,2'b0z,2'b1z : $display("Error in SEL");
15    endcase
16  endmodule
```



The conditional statement **case**

- Verilog case statement does an identity comparison (like the `==` operator)
 - One can use the case statement to check for logic `x` and `z` values as shown in the example below.

```
1 module case_xz(enable);  
2   input enable;  
3  
4   always @ (enable)  
5   case(enable)  
6     1'bz : $display ("enable is floating");  
7     1'bx : $display ("enable is unknown");  
8     default : $display ("enable is %b",enable);  
9   endcase  
10  endmodule
```



The conditional statement `case` and `casez`

- They are special versions of the case statement allow the x and z logic values to be used as “don't care”.
 - `casez`: Treats `z` as don't care.
 - `casex`: Treats `x` and `z` as don't care.



The conditional statement `case` and `casez`

```
1 module case_compare;  
2   reg sel;  
3  
4   always @ (sel)  
5     case (sel)  
6       1'b0 : $display("Normal : Logic 0 on sel");  
7       1'b1 : $display("Normal : Logic 1 on sel");  
8       1'bx : $display("Normal : Logic x on sel");  
9       1'bz : $display("Normal : Logic z on sel");  
10    endcase
```



The conditional statement **casex** and **casez**

```
11 always @ (sel)
12 casex (sel)
13     1'b0 : $display("CASEX : Logic 0 on sel");
14     1'b1 : $display("CASEX : Logic 1 on sel");
15     1'bx : $display("CASEX : Logic x on sel");
16     1'bz : $display("CASEX : Logic z on sel");
17 endcase
18
19 always @ (sel)
20 casez (sel)
21     1'b0 : $display("CASEZ : Logic 0 on sel");
22     1'b1 : $display("CASEZ : Logic 1 on sel");
23     1'bx : $display("CASEZ : Logic x on sel");
24     1'bz : $display("CASEZ : Logic z on sel");
25 endcase
```



The conditional statement `case` and `casez`

```
26 initial begin
27     #1 $display ("\n Driving 0");
28     sel = 0;
29     #1 $display ("\n Driving 1");
30     sel = 1;
31     #1 $display ("\n Driving x");
32     sel = 1'bx;
33     #1 $display ("\n Driving z");
34     sel = 1'bz;
35     #1 $finish;
36 end
37 endmodule
```



The conditional statement `case` and `casez`

Driving 0

Normal : Logic 0 on sel
CASEX : Logic 0 on sel
CASEZ : Logic 0 on sel

Driving 1

Normal : Logic 1 on sel
CASEX : Logic 1 on sel
CASEZ : Logic 1 on sel

Driving x

Normal : Logic x on sel
CASEX : Logic 0 on sel
CASEZ : Logic x on sel

Driving z

Normal : Logic z on sel
CASEX : Logic 0 on sel
CASEZ : Logic 0 on sel



The looping statement **forever**

- The **forever** loop executes continually, the loop never ends.
 - Normally we use forever statements in initial blocks.

```
1 module forever_example ();
2 reg clk;
3 initial begin
4     #1  clk = 0;
5     forever begin
6         #5  clk = ! clk;
7     end
8 end
9 initial begin
10     $monitor ("Time = %d  clk = %b", $time, clk);
11     #100 $finish;
12 end
13 endmodule
```



The looping statement **repeat**

- The **repeat** loop executes statements a fixed number of times.

```
1 module repeat_example();  
2 reg [3:0] opcode; reg [15:0] data; reg temp;  
3 always @ (opcode or data) begin  
4     if (opcode == 10) begin  
5         // Perform rotate  
6         repeat (8) begin  
7             #1 temp = data[15];  
8             data = data << 1;  
9             data[0] = temp;  
10        end  
11    end  
12 end  
13 endmodule
```



The looping statement **while**

- The **while** loop executes as long as the statement evaluates as true.

```
1 module while_example();  
2 reg [5:0] loc; reg [7:0] data;  
3 always @ (data or loc) begin  
4     loc = 0;  
5     if (data == 0) loc = 32;  
6     else begin  
7         while (data[0] == 0) begin  
8             loc = loc + 1;  
9             data = data >> 1;  
10        end  
11    end  
12    $display ("DATA = %b    LOCATION = %d",data,loc);  
13 end  
14 endmodule
```



The looping statement **for**

- The **for** loop is the same as the for loop used in any other programming language.
 - Executes an *initial assignment* once at the start of the loop.
 - Executes the loop as long as an *expression* evaluates as true.
 - Executes a *step assignment* at the end of each pass through the loop.

```
1 module for_example();  
2 integer i; reg [7:0] ram [0:255];  
3 initial begin  
4     for (i = 0; i < 256; i = i + 1) begin  
5         ram[i] <= 0; // Initialize the RAM with 0  
6         #1 $display(" Address = %g   Data = %h",i,ram[i]);  
7     end  
8     #1 $finish;  
9 end  
10 endmodule
```

